



Viewer License Agreement

You Must Read This License Agreement Before Proceeding.

This Scroll Wrap License is the Equivalent of a Shrink Wrap ⇒ Click License,
A Non-Disclosure Agreement that Creates a “Cone of Silence”.

By viewing this Document you **Permanently Release All Rights** that would allow you to restrict the **Royalty Free Use** by anyone implementing in Hardware, Software and/or other Methods in whole or in part what is Defined and Originates here in this Document. This Agreement particularly **Enjoins** the viewer from: Filing any **Patents** (À La Submarine) on said **Technology & Claims** and/or the use of any **Restrictive Instrument** that prevents anyone from using said **Technology & Claims** Royalty Free and without any Restrictions. This also applies to filing any **Trademarks** including but not limited to those being marked with “™” that Originate within this Document. **Trademarks** that Originate here belong to the **Author** of this Document unless otherwise noted. Transferring said **Technology** and/or **Claims** defined here without this Agreement to another Entity for the purpose of but not limited to allowing that Entity to circumvent this Agreement is Forbidden and will NOT release the Entity or the Transfer-er from Liability. Failure to Comply with this Agreement is **NOT** an Option if access to this content is desired. This Document contains **Technology & Claims** that are a **Trade Secret: Proprietary & Confidential** and cannot be transferred to another Entity without that Entity agreeing to this “Non-Disclosure Cone of Silence” **V.L.A.** Wrapper. Combining other Technology with said **Technology** and/or **Claims** is an acknowledgment by the Viewer that [s]he is automatically placing other Technology under the Licenses listed below making this License Self-Enforcing under an agreement of Confidentiality protected by this Wrapper.

The contents of/and this Document are released under following licenses so long as this Agreement remains attached to any and all files, papers, etc... that contain any said **Technology** and/or **Claims**. Any Hardware manufactured with said **Technology** and/or **Claims** must contain a brief message, e.g. “**V.L.A.** This Hardware contains Technology and/or Claims that are Licensed for Unrestricted and Royalty Free Use. Any knowledge gained by viewing this hardware design may not be used to interfere with the manufacture, sale and use of this hardware”.

Software only: [GNU General Public License 3.0 \(GPL\)](#)

Hardware (w/ || w/o software): Tucson Arizona Packet Radio TAPR [PDF](#) [ODT](#) [TXT](#)

This Document: [Creative Commons \(CC-BY\)](#)

Scrolling past this **1st** page is **The Point of No Return** and Acknowledges that You have Agreed to the Terms above. If you are Unable or Unwilling to Agree to these Terms then Close this Document.

**Trade Secret:
Proprietary
& Confidential**

This Document may be hosted anywhere and freely distributed without restriction.


Check out: [100mW TX Mono 1610AM](#) Transmitter article.

C-QUAM® & C-ISB™ AM Stereo Exciter


Generating a C-QUAM or C-ISB™ signal requires some pre-processing to produce a quality signal. Bandpass filtering, harmonic phase shifting, pre-emphasis, dynamic limiting, matrixing to name most of them. The following are schematic drawings for the various processes needed to prep the signal for the C-QUAM/C-ISB™ modulator. The modulator has an output section that will produce a composite output or the PM output at TTL & low level 100mV square waves along with L+R audio for the AM component for transmitter interface. The L+R audio also contains a DC component representing the '1+' carrier level providing a DC coupled output. Audio output impedance is 600Ω and is level adjustable to +12½dBm. Linear QuAM & ISB output modes are readily available for composite output by connecting the composite output driver to the output tank of the carrier, I & Q modulators instead of to the output tank of the C-QUAM modulator. For the separate AM & PM components the PM is readily available but the AM component must be recovered from the QuAM output with a pseudo-synchronous detector.

NOTE: When referring to I & Q this is synonymous with [1+]L+R & L-R respectively.


The first image is the input section. For common mode rejection a balun op-amp is used. The input is a ¼” stereo phone jack and in relation to stereo use the tip for Left is (+), the middle ring for Right is (–) and the base ring is ground. If a mono ¼” plug is plugged into it then the contact for the middle ring (–) will be grounded and will convert the input to un-balanced. Next are the 2nd order Chebyshev & 3rd order Butterworth high pass filters at ~50Hz with a combined 30dB/Oct. attenuation and finally the 2nd order Chebyshev low pass filter at ~10kHz (selectable 5, 7³/₅, 9, 10, 12³/₄) with 12dB/Oct. attenuation. A Chebyshev response is used here with a slight boost and in combination with a 3rd order Bessel low pass filter with a similar cutoff frequency later in the processing will simulate a good 5th order Butterworth low pass filter response. For both these filters other component values are specified for different cutoff frequencies.

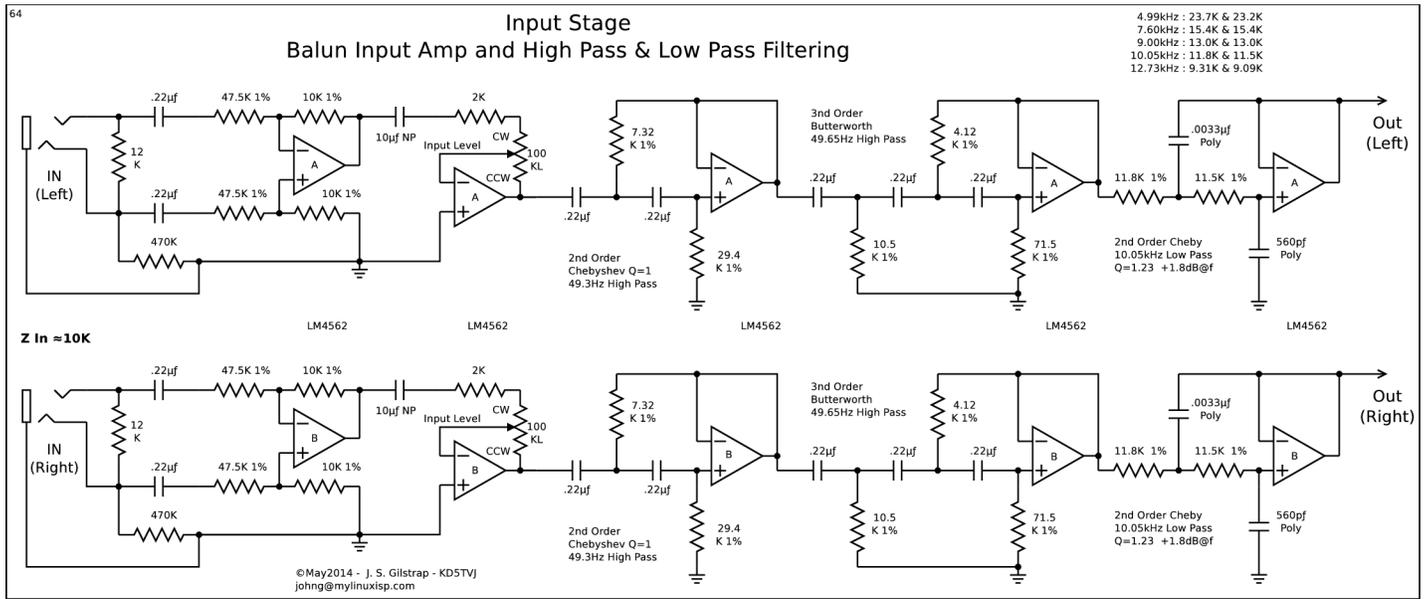


This next drawing is a phase shift network. When an ISB signal is generated phase shift networks similar to these are used to produce a rolling differential phase shift of 90° between L+R & L–R. A beneficial side effect is that this phase distortion which is un-noticeable to the human ear shifts the harmonics off the peaks of the fundamentals reducing peak amplitude but not volume level allowing for increased modulation level. Here the phase shift is the same for both channels and provides a fairly even rolling phase shift across most of the audio passband with a maximum of ~46°/oct. from 300Hz to 3kHz. Depending on programming material and audio bandwidth different frequencies could be used to produce an optimized response. This is not required for C-QUAM but can be beneficial. While C-ISB mode already provides a differential phase shift adding this may also reduce peak modulation levels further.

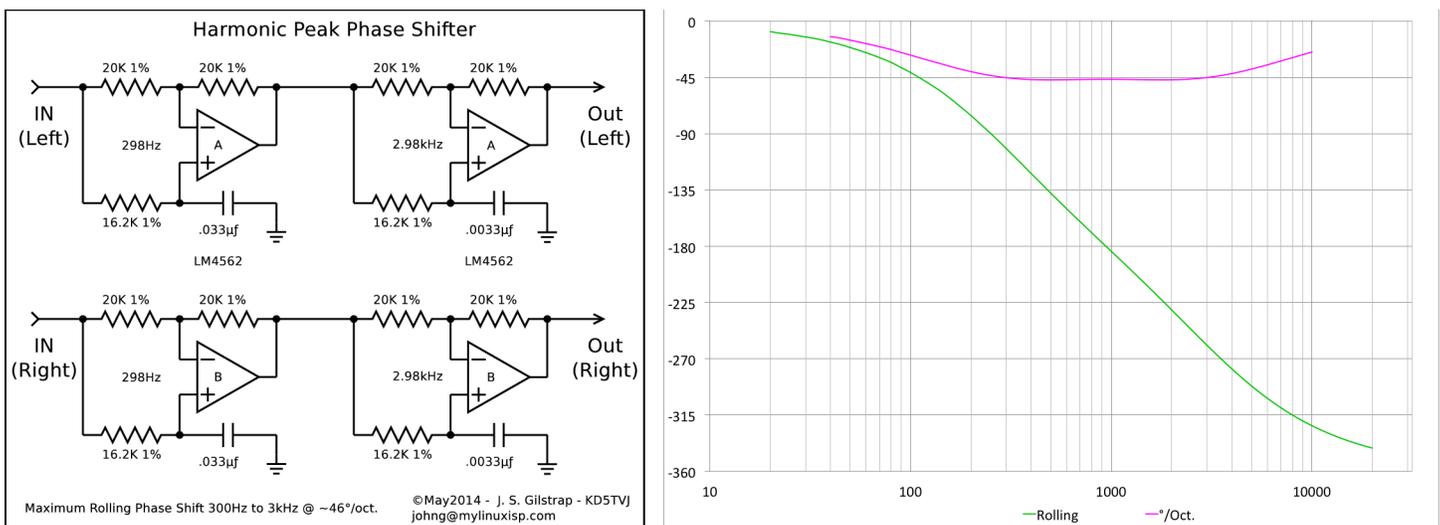


The next image is the pre-emphasis network with a $\sim 75\mu\text{s}$ response and a pole at 18.06kHz with a dynamic peak clipper afterwards. While the standard pre-emphasis has the pole at 8.7kHz this has been extended higher up to compensate for the gradual roll off of the higher frequencies created by the bandpass tanks in the modulators to approximate the 8.7kHz pole. There is also a bass de-emphasis applied to allow more headroom for mid and high frequency modulation levels. It starts at $\sim 60\text{Hz}$ and levels off at $\sim 180\text{Hz}$. The bass frequencies are usually the strongest in the signal and rob much of the headroom from the rest of the signal and is the least affected by noise. This $\sim 9\text{dB}$ attenuation at $\sim 60\text{Hz}$ is mild compared to the RIAA curve applied to vinyl records and can be compensated using the bass control on most receivers or the use of bass heavy headphones. To defeat this replace the $0.1\mu\text{f}$ capacitor with a $1\mu\text{f}$ NP. The Dynamic peak clipper has an attack time of $< 1\text{ms}$ and is defined by the 330Ω resistor charging the $2.2\mu\text{f}$ capacitors. The decay time is set by the 150K resistors in relation to the $2.2\mu\text{f}$ capacitors. The 3.3K & 22K resistor attenuation network that defines headroom helps to minimize over clipping during initial capacitor charging during initial signal response and can be adjusted by changing the value of the 22K . All three of these parameters can be adjusted for optimal performance. The clipper is placed after the pre-emphasis here but the most ideal place for it may be after all filtering but somewhere just before final Bessel low pass filter.

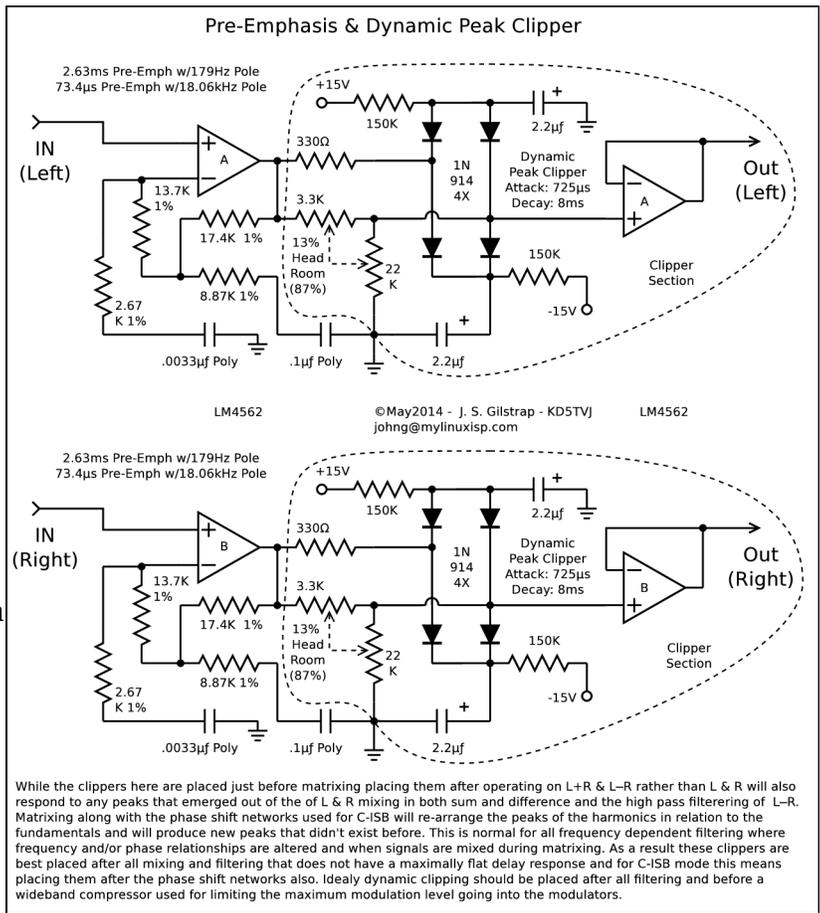

This next drawing is the matrixing of L & R into L+R & L-R and a high pass filter for L-R. This 2nd order high pass filter with a Q of $\frac{1}{2}$ has a complimentary all pass phase shift network that applies an equal but opposite phase shift to cancel out the phase shift of the high pass filter to produce a 0° phase shift high pass filter response. If C-ISB mode is used then to optimize sideband separation increasing L-R by $\sim 1\frac{1}{2}\text{dB}$ will help reduce 2nd order harmonics on the opposite sideband during average modulation levels. This can be done by replacing the 20K resistors with 16.8K s or placing 105K s in parallel with the 20K s. The receiver will need to have a $1\frac{1}{2}\text{dB}$ gain reduction applied also.

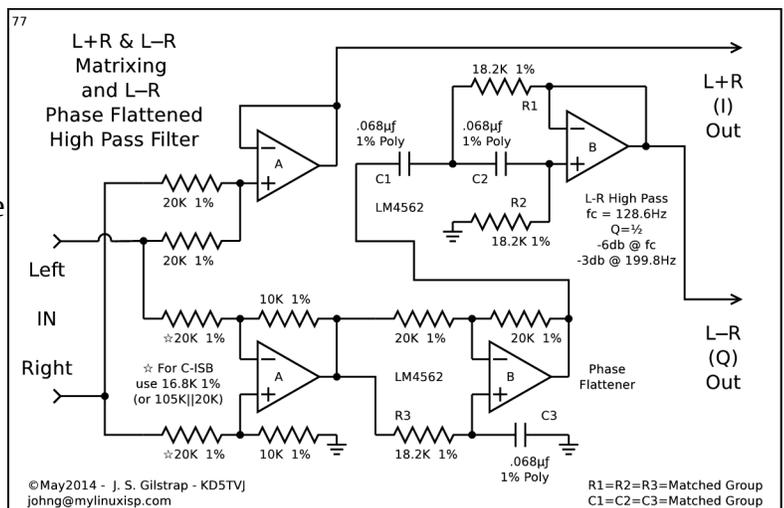


The next image is the block diagram flow chart. It shows all the processes in a sequence. The sequence can vary somewhat depending on several goals and whether it is in C-QUAM or C-ISB™ operation. For C-QUAM the actual gain reduction for the over easy compression is best applied to the separate L & R channels prior to matrixing but sensing for compressor control should be obtained after matrixing. For C-ISB™ while applying the gain reduction before matrixing may offer better single channel control during heavy single channel modulation good results can be obtained when gain reduction is done after matrixing offering more of a stereo expansion effect.

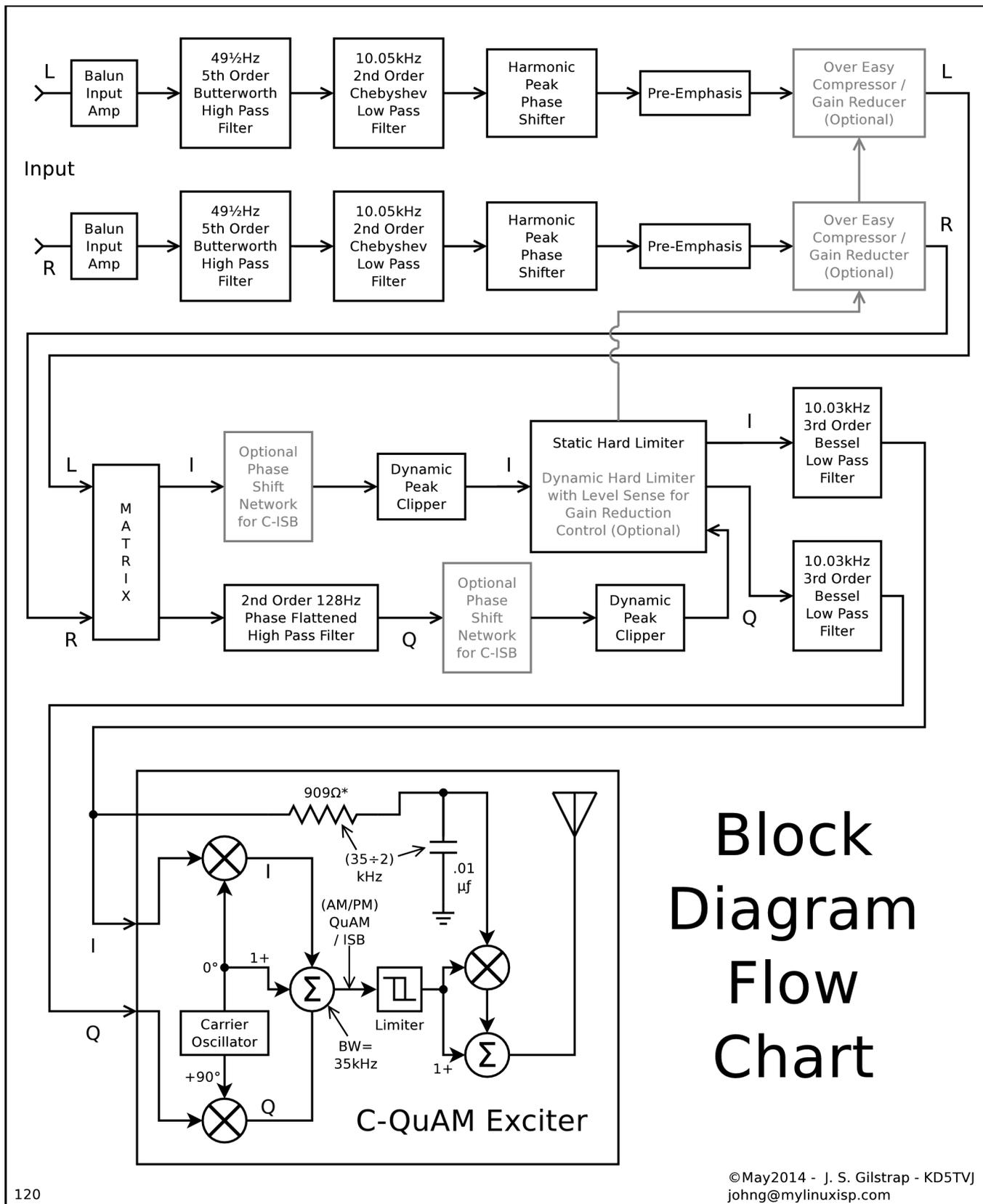

Suggested optimal order after input section. [C-]QUAM: Harmonic Phase Shift Networks, Pre-Emphasis, Gain Reduction / Over Easy Compression, Matrix, L-R High Pass Filter, Dynamic Peak Clipper, Dynamic Hard Limiter with Level Sense for Compressor, Matched Bessel Low Pass Filters. [C-]ISB: Harmonic Phase Shifter, Pre-Emphasis, Matrix, L-R high Pass Filter, [C-]ISB Phase Shift Networks, Dynamic Peak Clipper, Gain Reduction / Over Easy Compression on I & Q Stereo, Static Hard Limiter || Dynamic Hard Limiter with Level Sense for Compressor, Matched Bessel Low Pass Filters.

In the top half of this image is the PSN for [C-]ISB transmission and is placed after the matrix and L-R high pass filter. This is a three stage phase lagging network for transmission.


3 Stage Phase Shift Networks

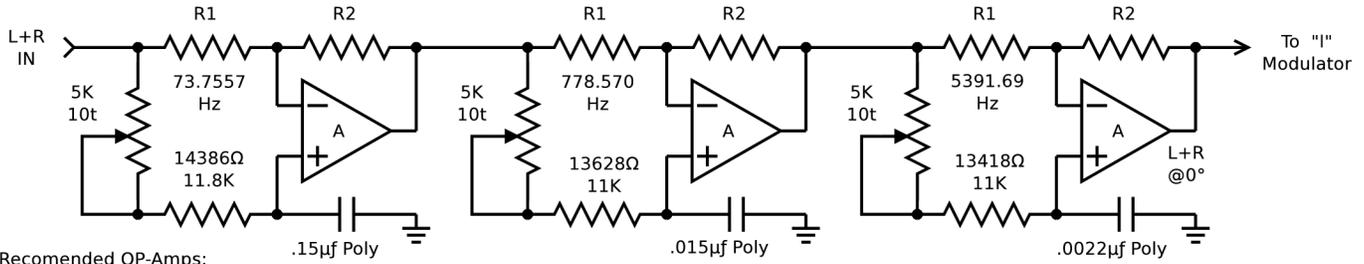

Recommended OP-Amps:
LM4562A
OPA2134
TL072


I & Q PSN for an Exciter

R1=R2 (10-20K)
Matched Pair or 1%

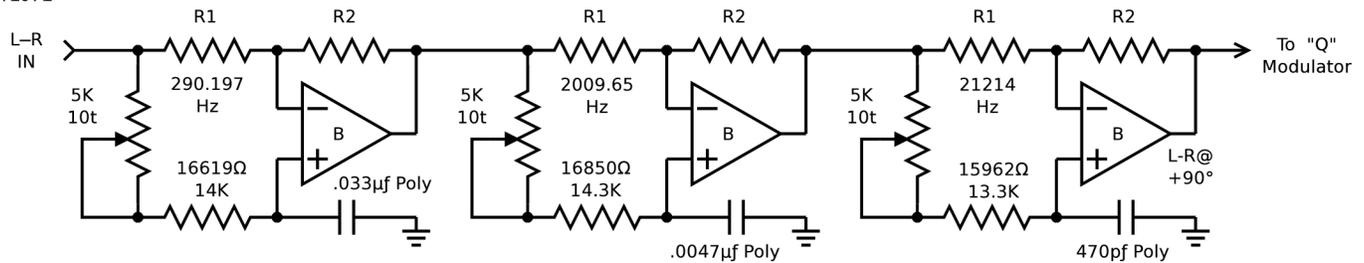

153Hz to 10¹/₄kHz -40db/±1.15° --- (-28db/4¹/₂° at 125Hz & 12¹/₂kHz)
(For ISB only. C-ISB will be less from Cosine Modulation)

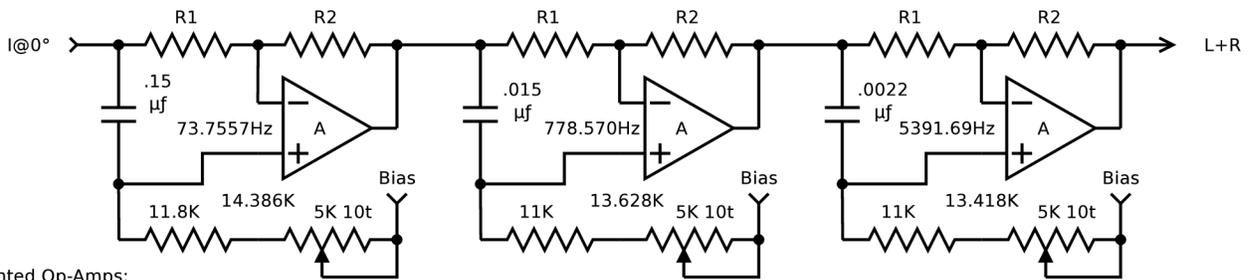
All Capacitors are Hi-Q
Temperature Stable
COG or NP0 Type
for Best Performance



Recommended Op-Amps:
TL072 (J-FET High Performance)
MC34072 (Low Voltage High Performance)
MC33172 (Low Voltage Low Power)

I & Q PSN for a Receiver


R1=R2 (10-20K)
Matched Pair or 1%

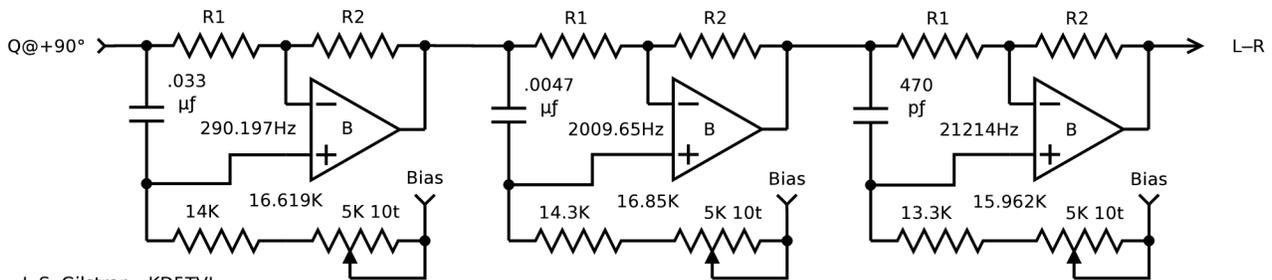

©2018 - J. S. Gilstrap - KD5TVJ
johng@mylinuxisp.com


In the bottom half of this image is the PSN for the receiver and is a 3 stage phase leading network using the same frequencies to return the signal's phase to its original state.

This 3 stage PSN has a -40dB opposite sideband suppression minimum from 153Hz to 10¹/₄kHz and at 125Hz & 12.5kHz it is still -28dB for ISB. C-ISB™ Cosine modulation will reduce this. If 2 independent non-stereo channels are used with (No C-) ISB then the 4 stage unit described in 'Discrete QuAM + ISB' could also be used for better sideband suppression but choosing this 3 stage is more economical making it a good standard for all TX/RX.

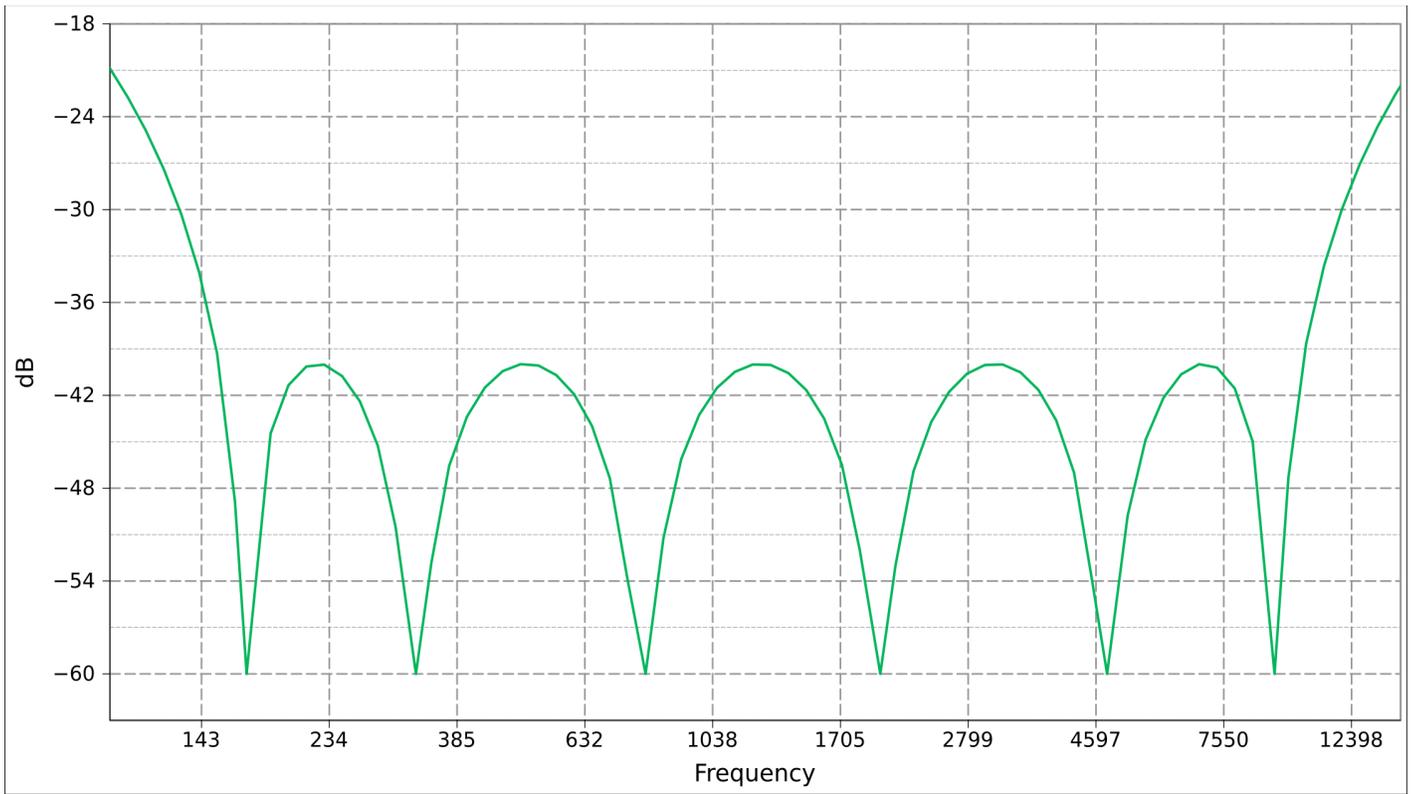


Above is the Opposite Sideband Suppression in dB vs Frequency for ISB.

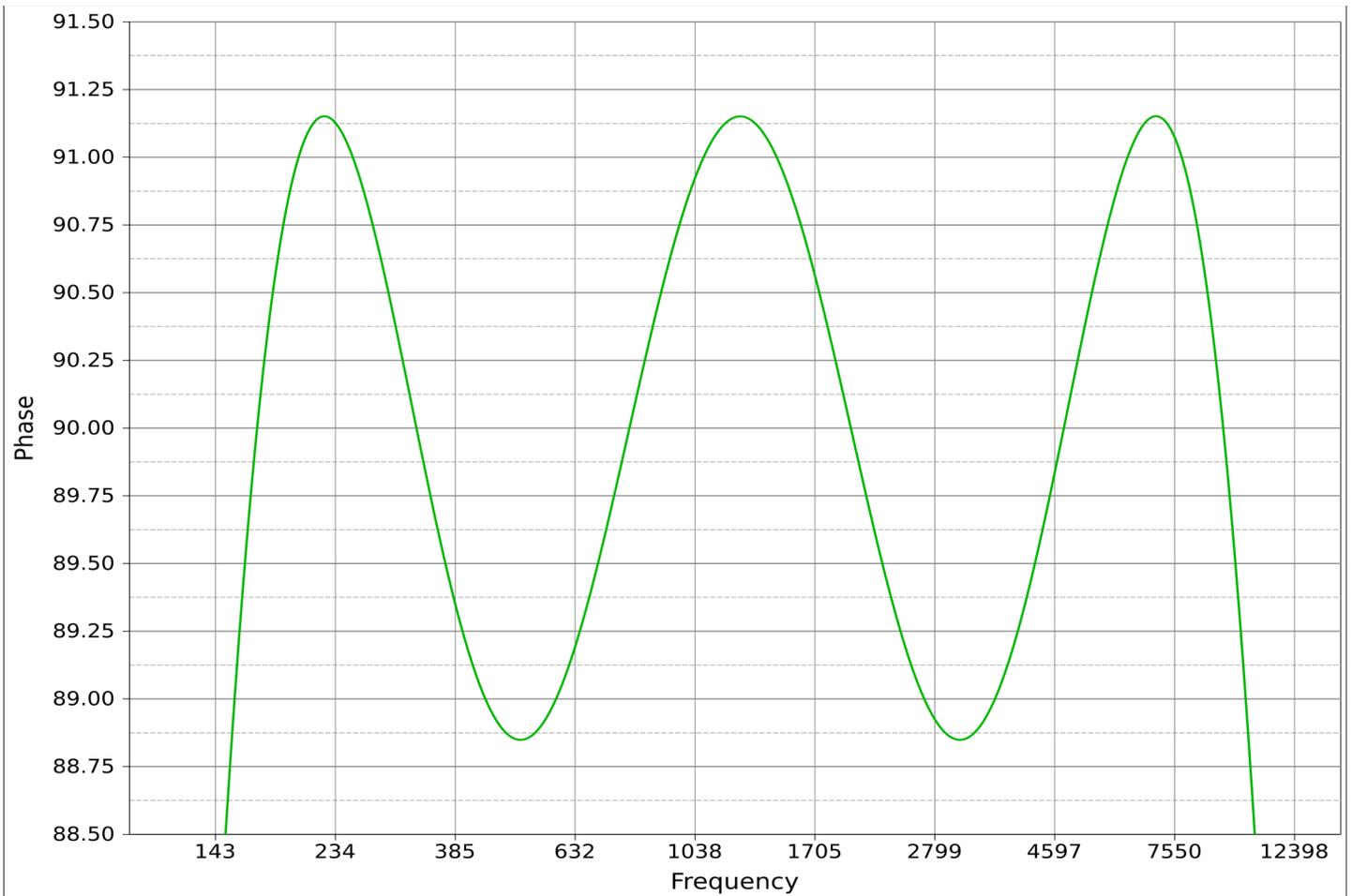
Below is the Differential Phase Shift between I & Q channels and Deviation away from 90°.



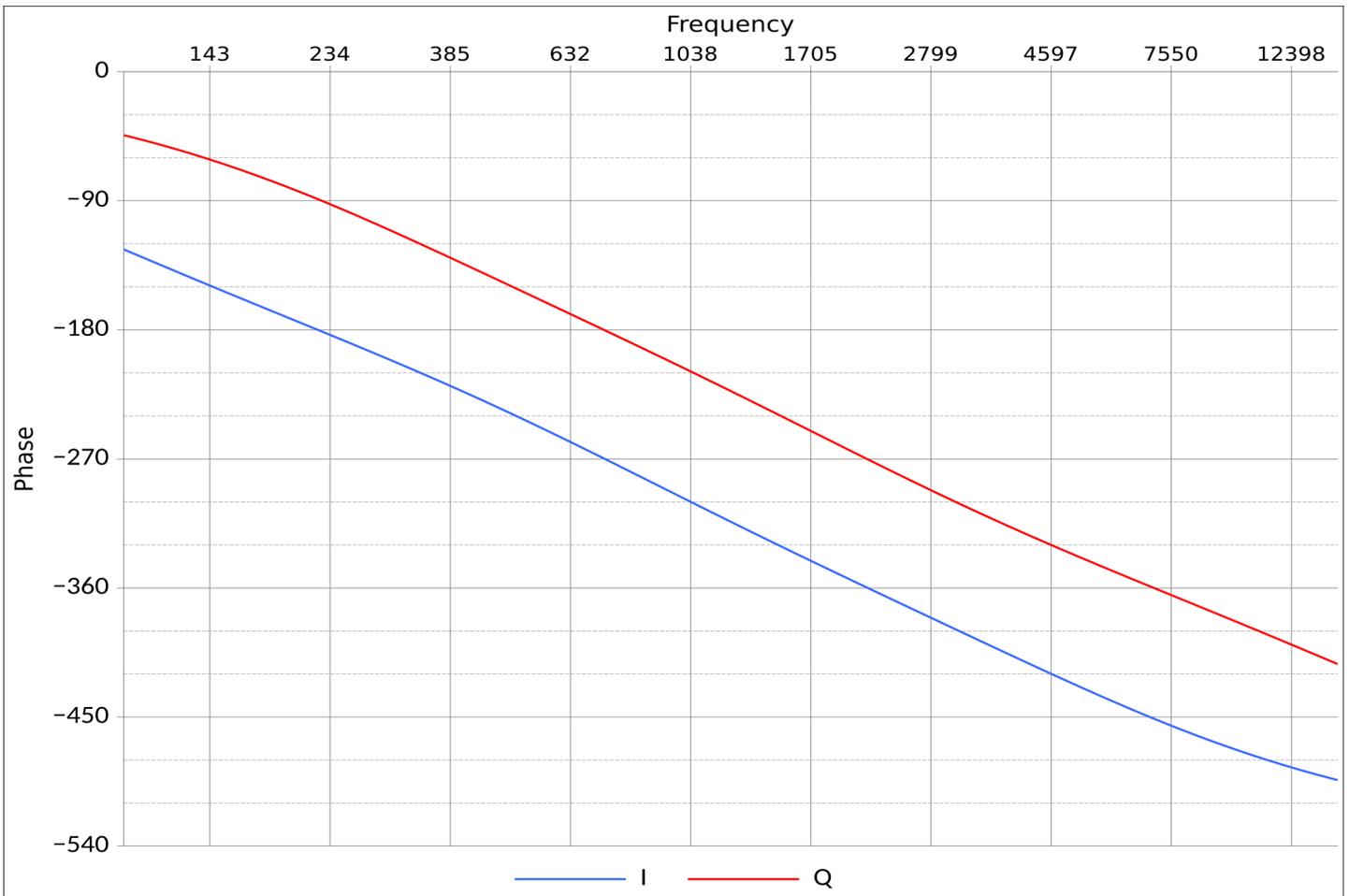
Phase Shift for I & Q Vectors providing a maximum $\sim 58^\circ/\text{Oct}$. Rolling Phase Shift.




This is the calibration tool to align the phase shift networks for both TX & RX. At its resonance each individual phasor will produce a 90° phase shift between its input and output. This detector will produce a voltage proportional to the deviation away from 90° . Using a DVM each phasor is calibrated when the meter reads 0.000V when the single sinusoidal frequency specified for it is injected into its input. The detector itself will need to be calibrated for 50% duty cycle on the final hex inverter outputs and tested first on a known sinusoidal quadrature signal. A 1Vp-p signal should produce full limiting with a fast rise and fall on the square wave.

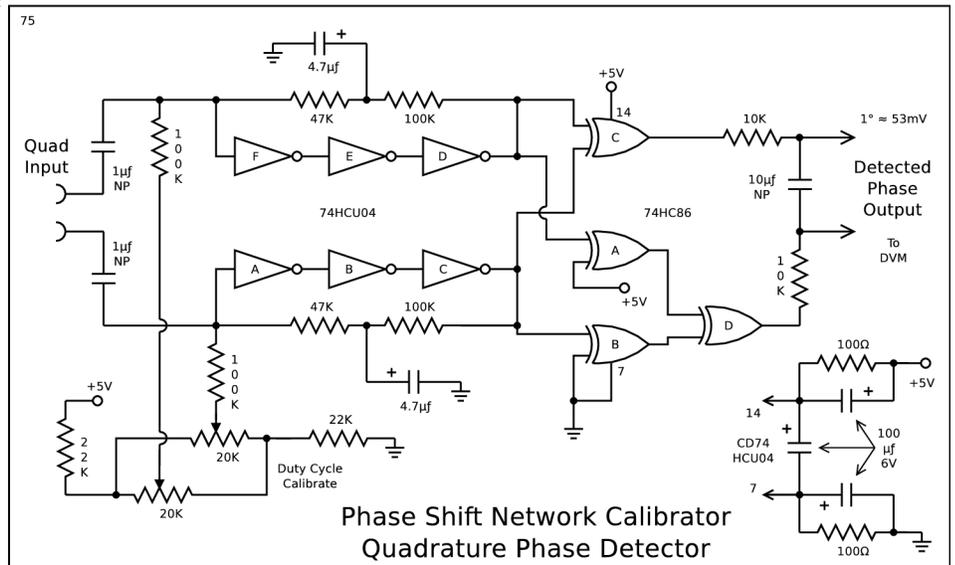

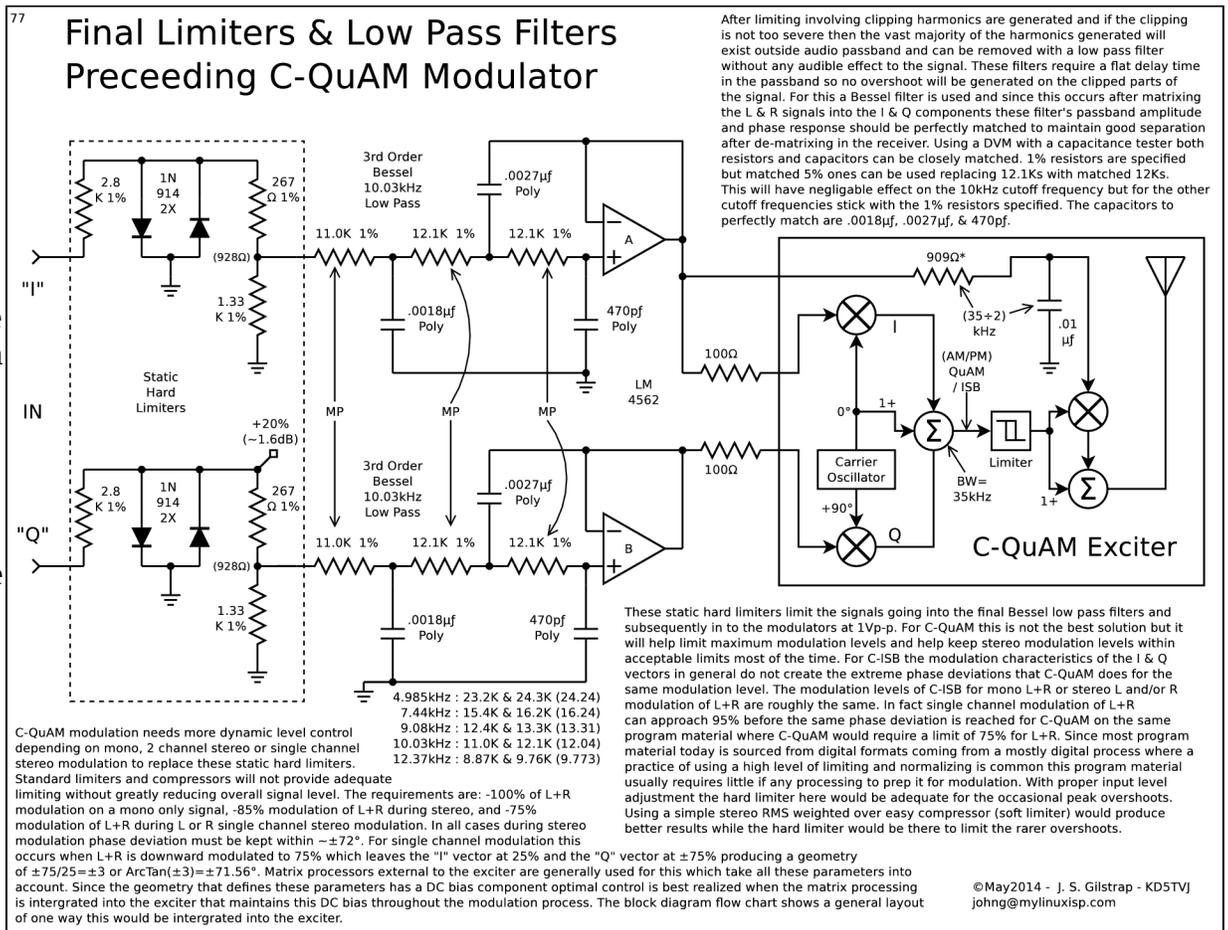
As an alternative to applying the +1½dB boost for C-ISB in the matrix circuit it may be more appropriate to apply it after the limiter as shown here, the +20% or ~1³⁄₅dB point. Connect the 11.0K resistor to it instead of where it is now.



Example Power Supply

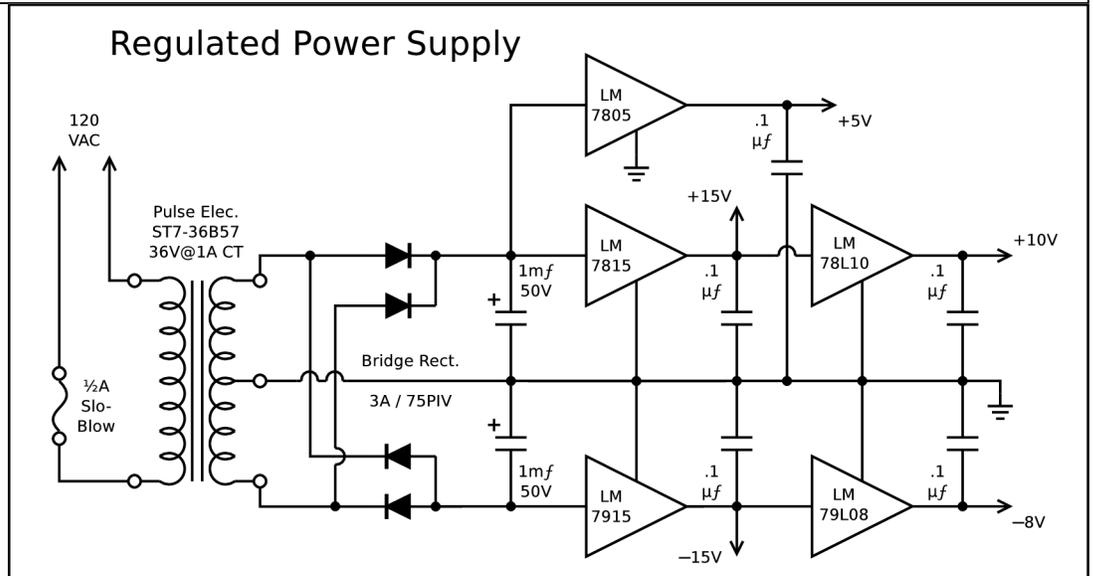

Output Section

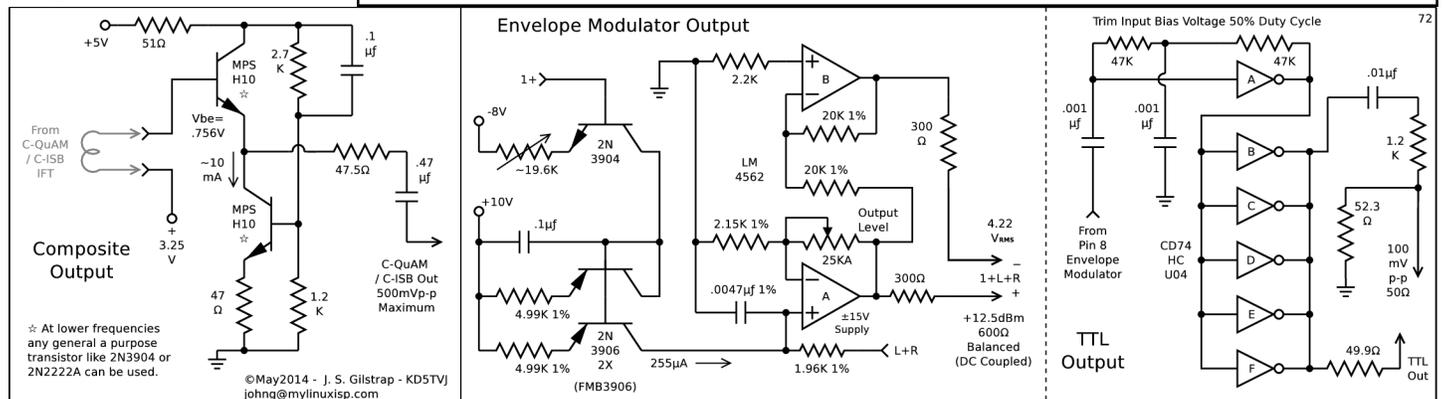

$$L2 = 1 / [(6\pi f)^2 \times C1] \quad \& \quad L1 = 1 / [(2\pi f)^2 \times C1] - L2$$

Exciter

To 1+L+R Envelope Modulator Output Stage


Optional Group Delay

L1 : L-43-1 AL=103
530kHz - 1050kHz

L1 : L-43-2 AL=88
1050kHz - 1700kHz

L2 : L-33-2 AL=61

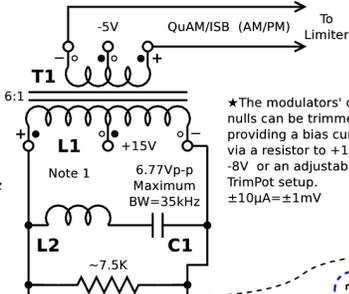Amidon Cores
Turns = $100 \times \sqrt{\mu H/AL}$
AL = $\mu H/100$ Turns




*The modulators' carrier nulls can be trimmed by providing a bias current via a resistor to +10V or -8V or an adjustable TrimPot setup. $\pm 10\mu A = \pm 1mV$

1. The primaries of the QuAM (T1) and C-QUAM (T2) tanks are the only tuned circuits and are made for the frequency of operation.

Different tanks can be made for different transmit frequencies. A series LC notch filter tuned to the 3rd harmonic has been integrated into the tanks but a notch for the 5th harmonic may also be needed.


In addition to a plugin circuit board with both tunable circuits the 4F carrier oscillator can be added also to the circuit board to make an easily pluggable method to switch transmit frequencies.

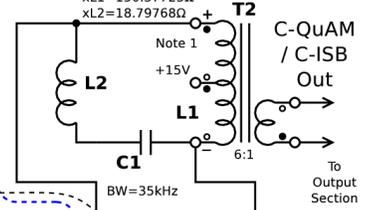F=Center Freq. (kHz)
Q=F/35, Rp=7.02K
At 'F':
xL1=169.16979Ω
xL2=150.37723Ω
xL2=18.79768Ω



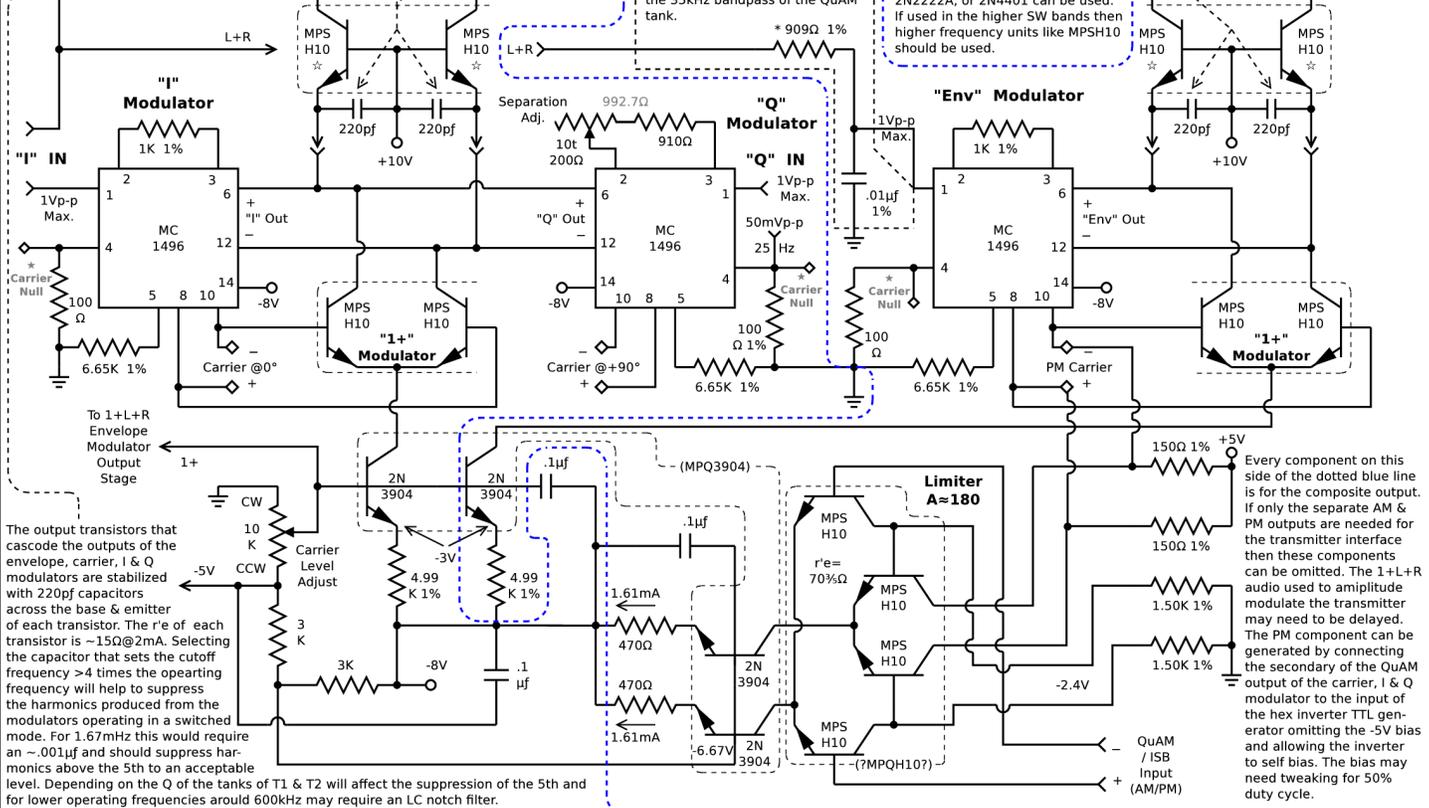
* 17.5kHz Low Pass to compliment the 35kHz bandpass of the QuAM tank.

☆ At lower frequencies any general purpose transistor like 2N3904, 2N2222A, or 2N4401 can be used. If used in the higher SW bands then higher frequency units like MPS10 should be used.




The output transistors that cascode the outputs of the envelope, carrier, I & Q modulators are stabilized with 220pf capacitors across the base & emitter of each transistor. The r'e of each transistor is ~15Ω@2mA. Selecting the capacitor that sets the cutoff frequency >4 times the operating frequency will help to suppress the harmonics produced from the modulators operating in a switched mode. For 1.67mHz this would require an ~.001μf and should suppress harmonics above the 5th to an acceptable level. Depending on the Q of the tanks of T1 & T2 will affect the suppression of the 5th and for lower operating frequencies around 600kHz may require an LC notch filter.

Every component on this side of the dotted blue line is for the composite output. If only the separate AM & PM outputs are needed for the transmitter interface then these components can be omitted. The 1+L+R audio used to amplitude modulate the transmitter may need to be delayed. The PM component can be generated by connecting the secondary of the QuAM output of the carrier, I & Q modulator to the input of the hex inverter TTL generator omitting the -5V bias and allowing the inverter to self bias. The bias may need tweaking for 50% duty cycle.

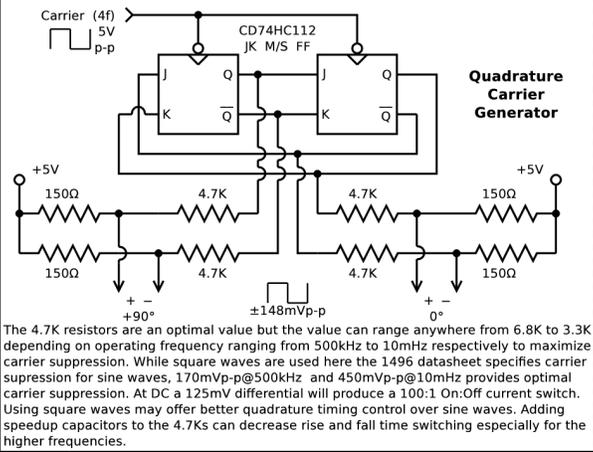

The 4.7K resistors are an optimal value but the value can range anywhere from 6.8K to 3.3K depending on operating frequency ranging from 500kHz to 10mHz respectively to maximize carrier suppression. While square waves are used here the 1496 datasheet specifies carrier suppression for sine waves, 170mVp-p@500kHz and 450mVp-p@10mHz provides optimal carrier suppression. At DC a 125mV differential will produce a 100:1 On:Off current switch. Using square waves may offer better quadrature timing control over sine waves. Adding speedup capacitors to the 4.7Ks can decrease rise and fall time switching especially for the higher frequencies.

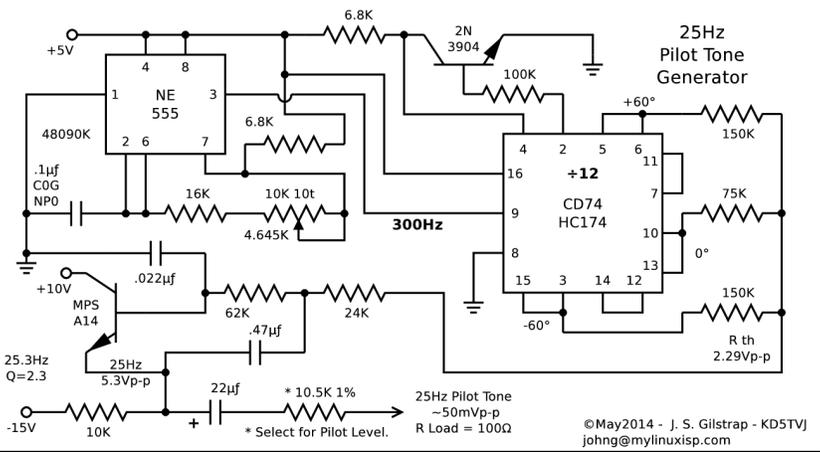


25.3Hz Q=2.3
25Hz 5.3Vp-p
22μf *10.5K 1%
25Hz Pilot Tone ~50mVp-p
R Load = 100Ω
* Select for Pilot Level.

A clock source at 4x the transmit frequency will need to be provided.

For C-ISB conversion of a C-QUAM decoder see: https://www.amstzone.org/QuadMod-4Way_13020.pdf

C-QUAM is a registered trademark of Motorola.

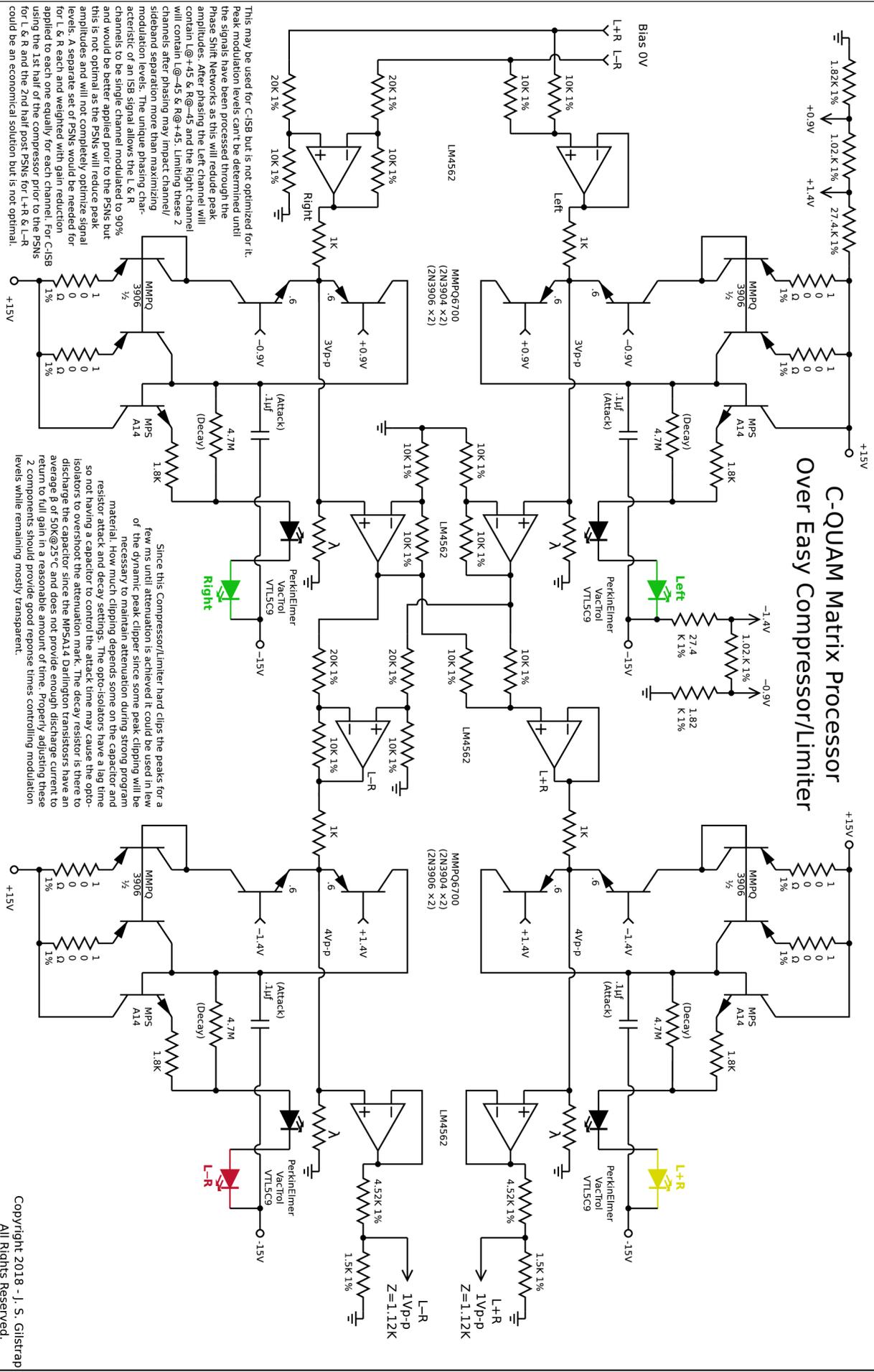C-QUAM Matrix Processor Over Easy Compressor/Limiter




This may be used for C-ISB but is not optimized for it. Peak modulation levels can't be determined until the signals have been processed through the Phase Shift Networks as this will reduce peak amplitudes. After phasing the Left channel will contain L@+45 & R@-45 and the Right channel will contain L@-45 & R@+45. Limiting these 2 channels after phasing may impact channel/sideband separation more than maximizing modulation levels. The unique phasing characteristic of an ISB signal allows the L & R channels to be single channel modulated to 90% and would be better applied prior to the PSNs but this is not optimal as the PSNs will reduce peak amplitudes and will not completely optimize signal levels. A separate set of PSNs would be needed for L & R each and weighted with gain reduction applied to each one equally for each channel. For C-ISB using the 1st half of the compressor prior to the PSNs for L & R and the 2nd half post PSNs for L+R & L-R could be an economical solution but is not optimal.

Since this Compressor/Limiter hard clips the peaks for a few ms until attenuation is achieved it could be used in lieu of the dynamic peak clipper since some peak clipping will be necessary to maintain attenuation during strong program material. How much clipping depends on the capacitor and resistor attack and decay settings. The opto-isolators have a lag time so not having a capacitor to control the attack time may cause the opto-isolators to overshoot the attenuation mark. The decay resistor is there to discharge the capacitor since the MPSA14 Darlington transistors have an average β of 50K@25°C and does not provide enough discharge current to return to full gain in a reasonable amount of time. Properly adjusting these 2 components should provide good response times controlling modulation levels while remaining mostly transparent.


To the right is a Phase Flattened Low Pass Filter. Use this if the out of band emissions exceed the transmission mask from heavy Stereo (L-R) modulation. It is tuned for a -3dB cutoff at $\sim 7\frac{1}{2}$ kHz although its corner frequency is above $11\frac{1}{2}$ kHz with a Q of $\frac{1}{2}$.

Both C-QUAM & C-ISB are non-linear multiplicative AM/PM modulation systems producing up to 6 times the modulating frequency in harmonics. Reducing the higher frequency content of L-R will reduce the out of band emissions to an acceptable level. The chosen cutoff frequency will depend on the high frequency content of the L-R program material and the amount of reduction of out of band emissions needed.

The corner frequency is determined by the 3 resistors chosen in conjunction with the 3 $.001\mu f$ capacitors using $1/(2\pi RC)$ and is 1.553... times higher than the -3dB point. There are 3 other cutoff frequencies specified and the resistors needed. The 3 capacitors and 3 resistors should be matched with each other or 1%. 15.0K resistors will produce a -3dB cutoff at ~ 6.83 kHz. Place this filter in the L-R path, pre or post of the complimentary high pass filter shown on page 4 in the matrix diagram. If using a dynamic limiter it may be more optimal to place it just prior to the Bessel Low Pass Filter on the Q (L-R) channel. This filter is not needed for QuAM or ISB since they are additive modulation systems of 2 AM waves in quadrature producing sidebands \pm the carrier reflective of their modulating signals.

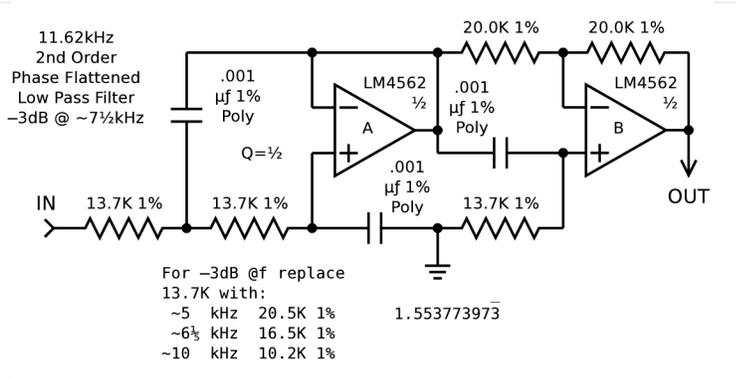

To the right is a more effective filtering scheme for the output tank circuits of the modulators in the exciter section. There are no emitter resistors and low pass filtering depends solely on the time constant created by $r'e$ and C. During light levels of modulation which creates changes in current through the emitters thus changing $r'e$, this in turn creates incidental phase modulation, which will mostly cancel out with the balanced push-pull arrangement. Under full modulation cancellation is far from complete and incidental phase modulation may create significant phase distortion especially if the cutoff frequency is not high enough above the transmit frequency. To minimize this emitter degeneration resistors are used that are $10\times$ of $r'e$ reducing total change in resistance to 10% of the change of $r'e$. A cutoff frequency of 3 to 4 times the transmit frequency should produce a flat enough response in both amplitude and group delay. The table lists suitable capacitors for a range of transmit frequencies. The capacitor values chosen are not critical, just that the cutoff frequency is somewhere between 3 and 4 times the transmit frequency. It might be able to go as low as $2\frac{1}{2}$ times the transmit frequency without any ill effects. Placing 1 or more ferrite beads on each of the resistors' leads will also help to reduce harmonics. A more robust solution is a balanced π filter preceding the resistors but this is a more complex design. This filtering may have an additional stabilizing effect on overall circuit performance reducing any undesirable parasitic effects.

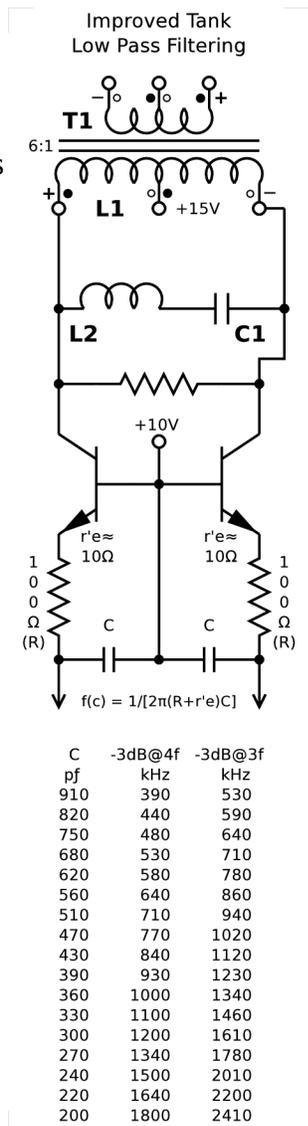

The exciter section is essentially broadband operating up into the lower portion of the SW band (<10 MHz). It is these tank sections that help define the frequency of operation and reduce the out of band emissions.

C-ISB™ conversion for the MC13028 AM Stereo decoder chip.

